

5152

B.Sc (Hons.) IN CSE, PART-I, 2ND SEMESTER EXAMINATION, 2018
DIGITAL SYSTEMS LAB
Subject Code: 510209

Time- 3 hours


Full Marks -- 40


[N.B. - Answer any two questions.]

1. Verify the operations of Basic gates.
- ✓ 2. Verify the operations of NAND gate as universal gate.
- ✓ 3. Implementation of NOR Gate using basic gates.
4. Verify the operation of XOR gate using basic gates.
5. Design and implementation of a Half Adder Circuit and verify its operation.
6. Design and implementation of a Full Adder Circuit and verify its operation.
7. Verify the operation of J – K Flip Flop.
8. Design and implementation of a 3 to 8 line decoder circuit using 74LS138 and verify its operation.
9. Design and implementation of a Half Subtractor circuit and verify its operations.
10. Design and implementation of an Asynchronous Counter.
11. Implementation of a Demultiplexer circuit.
12. Verify the operations of D/A Converter.

Marks Distribution:

Algorithm/Circuit Design	: 10
Coding/Circuit Construction	: 10
Result	: 10
Viva	: 10
<hr/>	
Total = 40	

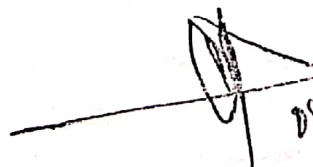
09.4.19


09.04.19